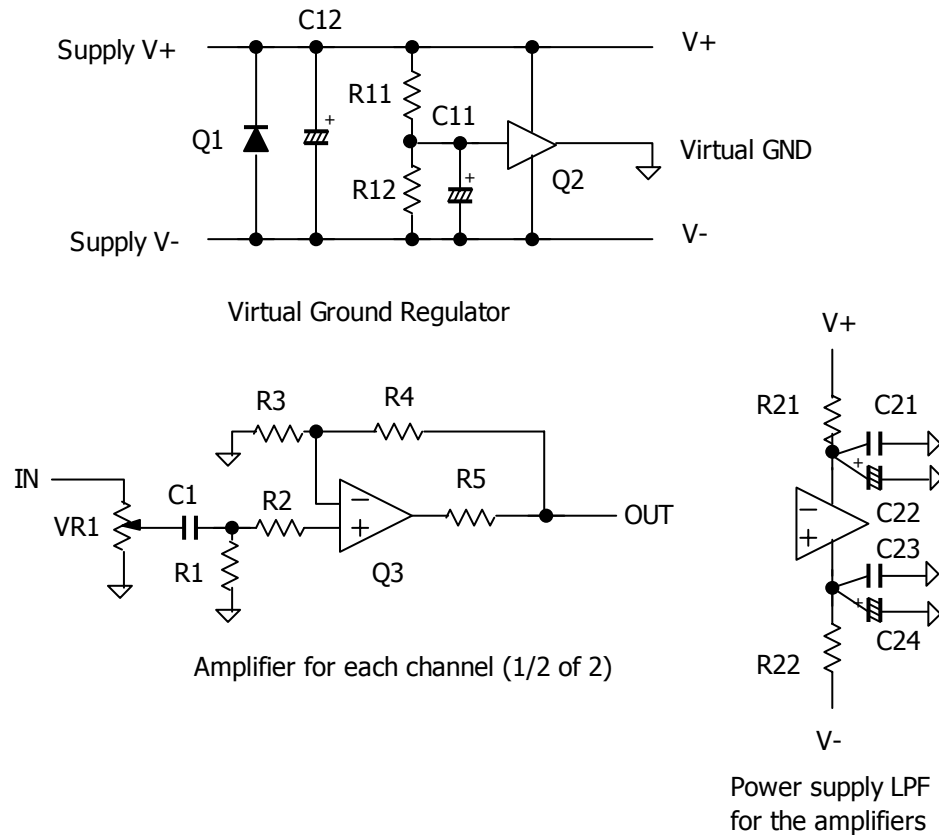


Chu-Moy-style Headphone Amplifier
by Kenji Rikitake <kenji.rikita@acm.org>
August 27, 2001

Schematics:



Parts Numbers and Values:

R1:	100kohm
R2:	1kohm
R3:	1kohm
R4:	4.7kohm
R5:	47ohm
R11:	10kohm
R12:	10kohm
R21:	47ohm
R22:	47ohm
VR1:	10kohm logarithmic (A-curve)
C1:	2.2uF Mylar
C11:	1uF 25V Electrolytic
C12:	1000uF 35V Electrolytic
C21:	0.1uF Ceramic
C22:	100uF 25V Electrolytic
C23:	0.1uF Ceramic
C24:	100uF 25V Electrolytic
Q1:	1N4002 (100V 1A Si Diode)
Q2:	Burr-Brown BUF634
Q3:	Burr-Brown OPA134 or 1/2 OPA2134

(All resistors are metal-film)